

# Assignment 3 : Structural Model

Ngo Van Canh

October 8, 2023

## Problem 1 : Write testbench for all problems in Assignment 2

### 1. Problem 1

---

```

1 module Problem1_tb;
2 reg[0:4] I;
3 wire F;
4 Problem1 p1(F, I[0], I[1], I[2], I[3]);
5 initial begin
6     for(I=0; I<16; I=I+1) begin
7         #5;
8         $display("%t I=%b F=%b", $time, I, F)
9     end
10
11 end
12 endmodule

```

---

Listing 1: Problem 1 testbench

Notice how the input I is defined to be 5 bits wide (line 2). This is to prevent the for loop (line 6) looping infinitely. Because if I is only 4bits, the variable itself never exceed 15. This is completely optional, alternatively, you can manually break the simulation at a desire time point, by typing the command "run 100" in the transcript command windows.

The above testbench should output something like following:

---

```

1 #           5 I=00000 F=1
2 #          10 I=00001 F=1
3 #          15 I=00010 F=0
4 #          20 I=00011 F=0
5 #          25 I=00100 F=1
6 #          30 I=00101 F=1
7 #          35 I=00110 F=1
8 #          40 I=00111 F=1
9 #          45 I=01000 F=0
10 #          50 I=01001 F=0
11 #          55 I=01010 F=0
12 #          60 I=01011 F=0
13 #          65 I=01100 F=0
14 #          70 I=01101 F=0
15 #          75 I=01110 F=0
16 #          80 I=01111 F=0

```

---

Listing 2: Problems 1 Testbench Output

## 2. 4-to-1 Multiplexer

---

```

1 module mux4_to_1_tb;
2 reg IN0, IN1, IN2, IN3;
3 reg S1, S0;
4 wire OUTPUT;
5 mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
6 initial begin
7     IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
8     #5 $display("%t IN0= %b, IN1= %b, IN2= %b, IN3= %b", $time, IN0, IN1, IN2,
9     IN3);
10    S1 = 0; S0 = 0;
11    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
12    S1 = 0; S0 = 1;
13    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
14    S1 = 1; S0 = 0;
15    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
16    S1 = 1; S0 = 1;
17    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
18 end
19 endmodule

```

---

Listing 3: 4-to-1 Multiplexer testbench

---

1 #	5 IN0= 1, IN1= 0, IN2= 1, IN3= 0
2 #	10 S1 = 0, S0 = 0, OUTPUT = 1
3 #	15 S1 = 0, S0 = 1, OUTPUT = 0
4 #	20 S1 = 1, S0 = 0, OUTPUT = 1
5 #	25 S1 = 1, S0 = 1, OUTPUT = 0

---

Listing 4: 4-to-1 Multiplexer Testbench Output

## 3. Half Adder

---

```

1 module half_adder_tb;
2 reg X, Y;
3 wire S, C;
4 half_adder ha(X, Y, S, C);
5 initial begin
6     $monitor($time, " X= %b, Y=%b, S= %b, C= %b", X, Y, S, C);
7 end
8 initial begin
9     #0 X=0; Y=0 ;
10    #5 X=0; Y=1;
11    #5 X=1; Y=0;
12    #5 X=1; Y=1;
13 end
14 endmodule

```

---

Listing 5: Half Adder testbench

---

1 #	0 X= 0, Y=0, S= 0, C= 0
2 #	5 X= 0, Y=1, S= 1, C= 0
3 #	10 X= 1, Y=0, S= 1, C= 0
4 #	15 X= 1, Y=1, S= 0, C= 1

---

Listing 6: Half Adder Testbench Output

## 4. Full Adder

```

1 module full_adder_tb;
2 reg X, Y, Ci;
3 wire S, Co;
4 full_adder fa(X, Y, Ci, S, Co);
5 initial begin
6     $monitor($time," X= %b, Y=%b, Ci= %b, S= %b, Co= %b", X, Y, Ci, S, Co);
7 end
8 initial begin
9     #0 X=0; Y=0; Ci=0;
10    #5 X=0; Y=0; Ci=1;
11    #5 X=0; Y=1; Ci=0;
12    #5 X=0; Y=1; Ci=1;
13    #5 X=1; Y=0; Ci=0;
14    #5 X=1; Y=0; Ci=1;
15    #5 X=1; Y=1; Ci=0;
16    #5 X=1; Y=1; Ci=1;
17 end
18 endmodule

```

Listing 7: Full Adder testbench

1 #	0 X= 0, Y=0, Ci= 0, S= 0, Co= 0
2 #	5 X= 0, Y=0, Ci= 1, S= 1, Co= 0
3 #	10 X= 0, Y=1, Ci= 0, S= 1, Co= 0
4 #	15 X= 0, Y=1, Ci= 1, S= 0, Co= 1
5 #	20 X= 1, Y=0, Ci= 0, S= 1, Co= 0
6 #	25 X= 1, Y=0, Ci= 1, S= 0, Co= 1
7 #	30 X= 1, Y=1, Ci= 0, S= 0, Co= 1
8 #	35 X= 1, Y=1, Ci= 1, S= 1, Co= 1

Listing 8: Full Adder Testbench Output

## 5. 4-bit Ripple Carry Adder

```

1 module Ripple_Carry_Adder_tb;
2 reg [3:0] X, Y;
3 reg Ci;
4 wire [3:0] S;
5 wire Co;
6 Ripple_Carry_Adder RCA(X, Y, Ci, S, Co);
7 initial begin
8     $monitor($time," X= %b, Y=%b, Ci= %b, S= %b, Co= %b", X, Y, Ci, S, Co);
9 end
10 initial begin
11    #0 X = 4'd0; Y = 4'd0; Ci = 1'b0;
12    #5 X = 4'd3; Y = 4'd4;
13    #5 X = 4'd2; Y = 4'd5;
14    #5 X = 4'd9; Y = 4'd9;
15    #5 X = 4'd10; Y = 4'd15;
16    #5 X = 4'd10; Y = 4'd5; Ci = 1'b1;
17 end
18 endmodule

```

Listing 9: 4-bit Ripple Carry Adder testbench

1 #	0 X= 0000, Y=0000, Ci= 0, S= 0000, Co= 0
2 #	5 X= 0011, Y=0100, Ci= 0, S= 0111, Co= 0
3 #	10 X= 0010, Y=0101, Ci= 0, S= 0111, Co= 0

---

```
4 #          15 X= 1001, Y=1001, Ci= 0, S= 0010, Co= 1
5 #          20 X= 1010, Y=1111, Ci= 0, S= 1001, Co= 1
6 #          25 X= 1010, Y=0101, Ci= 1, S= 0000, Co= 1
```

---

Listing 10: Full Adder Testbench Output

## Problem 2 : 8-to-3 Encoder and 3-to-8 Decoder

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

 
 


Figure 1: Encoder and Decoder

**Problem 3 : Flip-flops : D-FF, T-FF, JK-FF, SR-FF**

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

 


Figure 2: Flip-flops

*NOTE : Using structural model. Flip flops include reset signal.*