

## Assignment 3 : Structural Model

Ngo Van Canh

October 8, 2023

### Problem 1 : Write testbench for all problems in Assignment 2

#### 1. Problem 1

---

```
1 module Problem1_tb;
2 reg[0:4] I;
3 wire F;
4 // instantiate the design block
5 Problem1 p1(F, I[0], I[1], I[2], I[3]);
6 initial begin
7     I=0;
8     for(I=0; I<16; I=I+1) #5;
9 end
10
11 endmodule
```

---

Listing 1: Problem 1 testbench

#### 2. 4-to-1 Multiplexer

#### 3. Hald Adder

#### 4. Full Adder

#### 5. 4-bit Ripple Carry Adder

### Problem 2 : 8-to-3 Encoder and 3-to-8 Decoder

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

 


Figure 1: Encoder and Decoder

### Problem 3 : Flip-flops : D-FF, T-FF, JK-FF, SR-FF

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

 


Figure 2: Flip-flops

*NOTE : Using structural model. Flip flops include reset signal.*