

# Assignment 3 : Structural Model

Ngo Van Canh

October 8, 2023

## Problem 1 : Write testbench for all problems in Assignment 2

### 1. Problem 1

---

```
1 module Problem1_tb;
2 reg[0:4] I;
3 wire F;
4 Problem1 p1(F, I[0], I[1], I[2], I[3]);
5 initial begin
6     for(I=0; I<16; I=I+1) begin
7         #5;
8         $display("%t I=%b F=%b", $time, I, F)
9     end
10
11 end
12 endmodule
```

---

Listing 1: Problem 1 testbench

Notice how the input I is defined to be 5 bits wide (line 2). This is to prevent the for loop (line 6) looping infinitely. Because if I is only 4bits, the variable itself never exceed 15. This is completely optional, alternatively, you can manually break the simulation at a desire time point, by typing the command "run 100" in the transcript command windows (100 is the duration you want to run, change it to suit the simulation)

The above testbench should output something like following:

---

1	#	5	I=00000	F=1
2	#	10	I=00001	F=1
3	#	15	I=00010	F=0
4	#	20	I=00011	F=0
5	#	25	I=00100	F=1
6	#	30	I=00101	F=1
7	#	35	I=00110	F=1
8	#	40	I=00111	F=1
9	#	45	I=01000	F=0
10	#	50	I=01001	F=0
11	#	55	I=01010	F=0
12	#	60	I=01011	F=0
13	#	65	I=01100	F=0
14	#	70	I=01101	F=0
15	#	75	I=01110	F=0
16	#	80	I=01111	F=0

---

Listing 2: Problems 1 Testbench Output

## 2. 4-to-1 Multiplexer

---

```

1 module mux4_to_1_tb;
2 reg IN0, IN1, IN2, IN3;
3 reg S1, S0;
4 wire OUTPUT;
5 mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
6 initial begin
7     IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
8     #5 $display("%t IN0= %b, IN1= %b, IN2= %b, IN3= %b", $time, IN0, IN1, IN2,
9     IN3);
10    S1 = 0; S0 = 0;
11    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
12    S1 = 0; S0 = 1;
13    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
14    S1 = 1; S0 = 0;
15    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
16    S1 = 1; S0 = 1;
17    #5 $display("%t S1 = %b, S0 = %b, OUTPUT = %b", $time, S1, S0, OUTPUT);
18 end
19 endmodule

```

---

Listing 3: 4-to-1 Multiplexer testbench

---

1 #	5 IN0= 1, IN1= 0, IN2= 1, IN3= 0
2 #	10 S1 = 0, S0 = 0, OUTPUT = 1
3 #	15 S1 = 0, S0 = 1, OUTPUT = 0
4 #	20 S1 = 1, S0 = 0, OUTPUT = 1
5 #	25 S1 = 1, S0 = 1, OUTPUT = 0

---

Listing 4: 4-to-1 Multiplexer Testbench Output

### 3. Half Adder

```

1 module half_adder_tb;
2 reg X, Y;
3 wire S, C;
4 half_adder ha(X, Y, S, C);
5 initial begin
6     $monitor($time, " X= %b, Y=%b, S= %b, C= %b", X, Y, S, C);
7 end
8 initial begin
9     #0 X=0; Y=0 ;
10    #5 X=0; Y=1;
11    #5 X=1; Y=0;
12    #5 X=1; Y=1;
13 end
14 endmodule

```

Listing 5: Half Adder testbench

1 #	0 X= 0, Y=0, S= 0, C= 0
2 #	5 X= 0, Y=1, S= 1, C= 0
3 #	10 X= 1, Y=0, S= 1, C= 0
4 #	15 X= 1, Y=1, S= 0, C= 1

Listing 6: Half Adder Testbench Output

### 4. Full Adder

```

1 module full_adder_tb;
2 reg X, Y, Ci;
3 wire S, Co;
4 full_adder fa(X, Y, Ci, S, Co);
5 initial begin
6     $monitor($time, " X= %b, Y=%b, Ci= %b, S= %b, Co= %b", X, Y, Ci, S, Co);
7 end
8 initial begin
9     #0 X=0; Y=0; Ci=0;
10    #5 X=0; Y=0; Ci=1;
11    #5 X=0; Y=1; Ci=0;
12    #5 X=0; Y=1; Ci=1;
13    #5 X=1; Y=0; Ci=0;
14    #5 X=1; Y=0; Ci=1;
15    #5 X=1; Y=1; Ci=0;
16    #5 X=1; Y=1; Ci=1;
17 end
18 endmodule

```

Listing 7: Full Adder testbench

1 #	0 X= 0, Y=0, Ci= 0, S= 0, Co= 0
2 #	5 X= 0, Y=0, Ci= 1, S= 1, Co= 0
3 #	10 X= 0, Y=1, Ci= 0, S= 1, Co= 0
4 #	15 X= 0, Y=1, Ci= 1, S= 0, Co= 1
5 #	20 X= 1, Y=0, Ci= 0, S= 1, Co= 0
6 #	25 X= 1, Y=0, Ci= 1, S= 0, Co= 1
7 #	30 X= 1, Y=1, Ci= 0, S= 0, Co= 1
8 #	35 X= 1, Y=1, Ci= 1, S= 1, Co= 1

Listing 8: Full Adder Testbench Output

## 5. 4-bit Ripple Carry Adder

---

```

1 module Ripple_Carry_Adder_tb;
2 reg [3:0] X, Y;
3 reg Ci;
4 wire [3:0] S;
5 wire Co;
6 Ripple_Carry_Adder RCA(X, Y, Ci, S, Co);
7 initial begin
8     $monitor($time, " X= %b, Y=%b, Ci= %b, S= %b, Co= %b", X, Y, Ci, S, Co);
9 end
10 initial begin
11     #0 X = 4'd0; Y = 4'd0; Ci = 1'b0;
12     #5 X = 4'd3; Y = 4'd4;
13     #5 X = 4'd2; Y = 4'd5;
14     #5 X = 4'd9; Y = 4'd9;
15     #5 X = 4'd10; Y = 4'd15;
16     #5 X = 4'd10; Y = 4'd5; Ci = 1'b1;
17 end
18 endmodule

```

---

Listing 9: 4-bit Ripple Carry Adder testbench

---

1 #	0 X= 0000, Y=0000, Ci= 0, S= 0000, Co= 0
2 #	5 X= 0011, Y=0100, Ci= 0, S= 0111, Co= 0
3 #	10 X= 0010, Y=0101, Ci= 0, S= 0111, Co= 0
4 #	15 X= 1001, Y=1001, Ci= 0, S= 0010, Co= 1
5 #	20 X= 1010, Y=1111, Ci= 0, S= 1001, Co= 1
6 #	25 X= 1010, Y=0101, Ci= 1, S= 0000, Co= 1

---

Listing 10: Full Adder Testbench Output

## Problem 2 : 8-to-3 Encoder and 3-to-8 Decoder

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

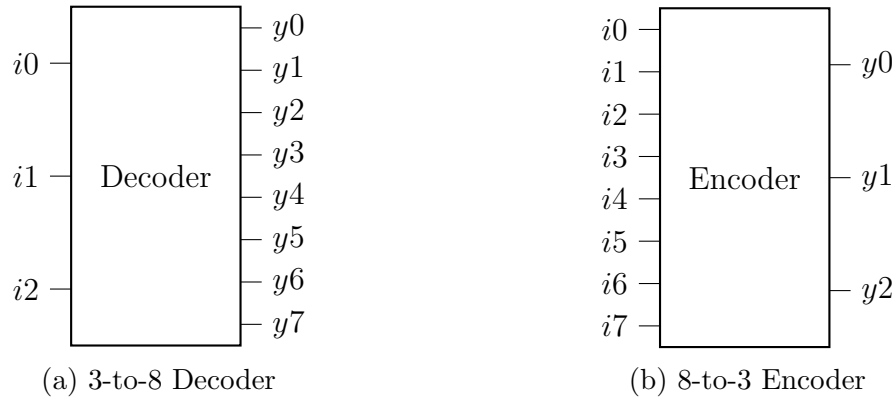


Figure 1: Encoder and Decoder

### a. Decoder

$i0$	$i1$	$i2$	$y0$	$y1$	$y2$	$y3$	$y4$	$y5$	$y6$	$y7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Table 1: Decoder 3-to-8 Truth Table

$$\Rightarrow \begin{cases} y0 = i0'i1'i2' \\ y1 = i0'i1'i2 \\ y2 = i0'i1i2' \\ y3 = i0'i1i2 \\ y4 = i0i1'i2' \\ y5 = i0i1'i2 \\ y6 = i0i1i2' \\ y7 = i0i1i2 \end{cases}$$

---

```
1 module Decoder_3_to_8 (  
2     input [0:2] i,  
3     output [0:7] y  
4 );  
5  
6  
7 endmodule
```

---

Listing 11: Decoder 3-to-8 and testbench

---

```
1 #  
2 #  
3 #  
4 #  
5 #  
6 #  
7
```

---

Listing 12: Full Adder Testbench Output

---

## b. Encoder

**Problem 3 : Flip-flops : D-FF, T-FF, JK-FF, SR-FF**

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

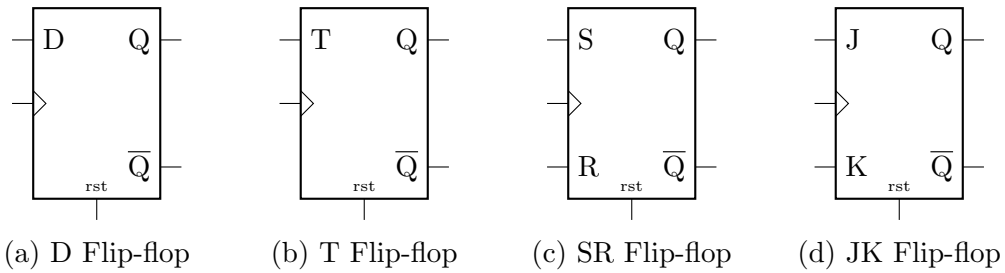


Figure 2: Flip-flops

*NOTE : Using structural model. Flip flops include reset signal.*