

## Assignment 3 : Structural Model

Ngo Van Canh

October 2, 2023

### **Problem 1 : Write testbench for all problems in Assignment 2**

1. Problem 1
2. 4-to-1 Multiplexer
3. Half Adder
4. Full Adder
5. 4-bit Ripple Carry Full Adder

### **Problem 2 : 8-to-3 Encoder and 3-to-8 Decoder**

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

### **Problem 3 : Flip Flops : T-FF, D-FF, JK-FF, SR-FF**

1. Construct truth table.
2. Determine output function.
3. Write Verilog code and testbench for that circuit.

*Note : Using structural model. Flip flops include reset signal.*