

Assignment 4

Ngo Van Canh

2023

Problem 1 : 16-bit Carry Look Ahead Adder

Write code Verilog: Design code and testbench code

NOTE : A 16-bit Carry Look Ahead Adder can be formed by cascading four 4-bit Carry Look Ahead Adder

Problem 2 : 4-bit Ripple Carry Counter

Write Verilog code and testbench. Simulate your design.

NOTE : Using T - flipflop (structural model) you designed in Assignment 3.

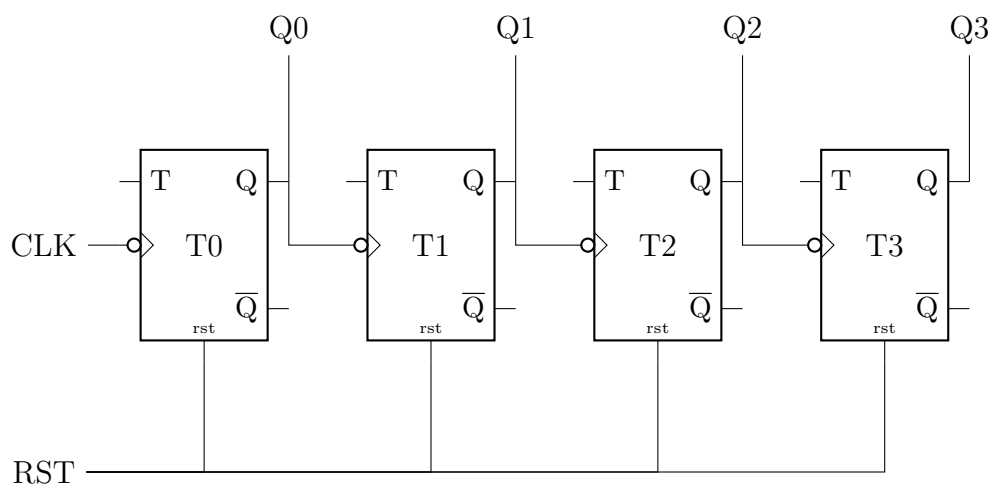


Figure 1: 4-bit Ripple Carry Counter

Problem 3 : 4-bit Gray Counter

Write code Verilog: Design code and simulation by testbench.

NOTE : Note: Using \$display syntax and screenshot waveform.

Problem 4 : BCD to 7 Segment Display Decoder

Write code Verilog: Design code and simulation by testbench.

