

Assignment 4

2023

Design code, testbench and simulation the following module

Problem 1 : 4-bit Ripple Carry Counter

NOTE : Using T - flipflop (Structural model) that you designed in Assignment 3.

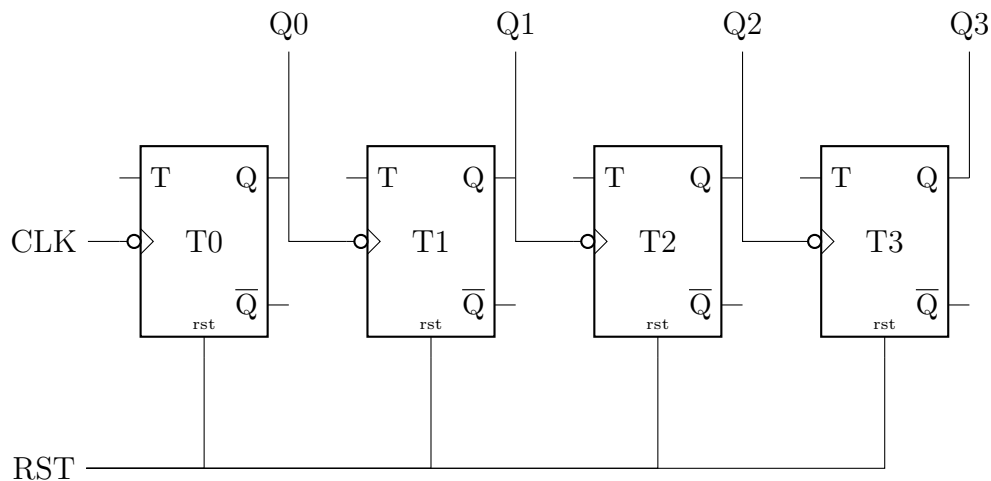


Figure 1: 4-bit Ripple Carry Counter

Problem 2 : 4-bit Gray Counter

NOTE : The counter has synchronous reset

Problem 3 : BCD to 7 Segment Display Decoder

